



Cairo University
Faculty of Engineering


Department of Electronics and
Communications Engineering
ELC 3060 – Spring 2023



Mini Project #1: Design and Implementation of a Biquad

Name: شهيرة اسامة شفيع محمد	Sec:2	BN:28	ID:9202725
-----------------------------	-------	-------	------------

DESIGN STEP (FIRST STEP):

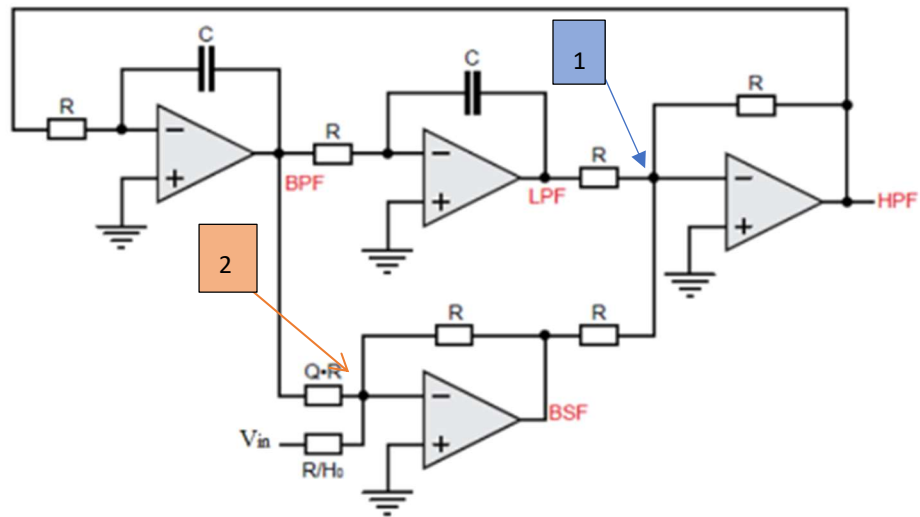

The BPF & LPF are integrators so:

$$\text{BPF} = \frac{-1}{sCR} \text{HPF} \quad \text{-----} \rightarrow (1)$$

$$\text{LPF} = \frac{-1}{sCR} \text{BPF} = \left(\frac{1}{sCR} \right)^2 \text{HPF} \quad \text{-----} \rightarrow (2)$$

By applying KCL at node 1:

$$\frac{\text{LPF}}{R} + \frac{\text{BSF}}{R} = \frac{-\text{HPF}}{R}$$

$$\text{LPF} + \text{BSF} = -\text{HPF} \quad \text{-----} \rightarrow (3)$$

By applying KCL at node 2:

$$\frac{\text{BPF}}{Q/R} + \frac{H_o V_{in}}{R} = \frac{-\text{BSF}}{R} \quad \text{-----} \rightarrow (4)$$

$$\frac{-1}{Q} \frac{1}{sCR} \text{HPF} + H_o V_{in} = \text{HPF} + \text{LPF}$$

$$\frac{-1}{Q} \frac{1}{sCR} \text{HPF} + H_o V_{in} = \text{HPF} \left[1 + \left(\frac{1}{sCR} \right)^2 \right]$$

$$\text{HPF} \left[\frac{1 + (sCR)^2}{(sCR)^2} \right] + \frac{1}{Q} \frac{1}{sCR} \text{HPF} = H_o V_{in}$$

$$\text{HPF} \left[\frac{SCR + Q(SCR)^2 + Q}{Q(SCR)^2} \right] = H_o \text{ Vin}$$

$$\frac{\text{HPF}}{\text{Vin}} = \frac{H_o Q (SCR)^2}{SCR + Q + (SCR)^2 Q} = \frac{H_o S^2}{S^2 + \frac{S}{CRQ} + \frac{1}{(CR)^2}} \quad \text{-----} \rightarrow (5) \quad (\text{HPF transfer function})$$

By substituting by Eqn (5) in Eqn (4)

$$\text{Vin} \left[-\frac{1}{Q} \frac{1}{SCR} \frac{H_o S^2}{S^2 + \frac{S}{CRQ} + \frac{1}{(CR)^2}} + H_o \right] = -\text{BSF}$$

$$H_o \left[\frac{S^2 + \frac{1}{(CR)^2} + \frac{S}{CRQ} - \frac{S}{CRQ}}{S^2 + \frac{S}{CRQ} + \frac{1}{(CR)^2}} \right] \text{Vin} = -\text{BSF}$$

$$-H_o \left[\frac{S^2 + \frac{1}{(CR)^2}}{S^2 + \frac{S}{CRQ} + \frac{1}{(CR)^2}} \right] = \frac{\text{BSF}}{\text{Vin}} \quad \text{-----} \rightarrow (6) \quad (\text{BSF transfer function})$$

By substituting by Eqn (5) in Eqn (2)

$$\text{Vin} \left[\frac{1}{(SCR)^2} \frac{H_o S^2}{S^2 + \frac{S}{CRQ} + \frac{1}{(CR)^2}} \right] = \text{LPF}$$

$$\frac{\text{LPF}}{\text{Vin}} = \left[\frac{\frac{H_o}{(CR)^2}}{S^2 + \frac{S}{CRQ} + \frac{1}{(CR)^2}} \right] \quad \text{-----} \rightarrow (7) \quad (\text{LPF transfer function})$$

By substituting by Eqn (5) in Eqn (1)

$$\text{BPF} = \left[\frac{-1}{SCR} \frac{H_o S^2}{S^2 + \frac{S}{CRQ} + \frac{1}{(CR)^2}} \right] \text{Vin}$$

$$\frac{\text{BPF}}{\text{Vin}} = \left[\frac{\frac{-H_o S}{RC}}{S^2 + \frac{S}{CRQ} + \frac{1}{(CR)^2}} \right] \quad \text{-----} \rightarrow (8) \quad (\text{BPF transfer function})$$

From characteristic Eqn :



$$\omega_o = \frac{1}{RC} \quad \& \quad f_o = 1\text{MHz}$$

Then RC = 0.159 μ


Assuming R = 1k Ω & C = 159 PF

SEMULATION STEP (SECOND STEP):

IDEAL OPAMP SCHEMATIC & SYMBOL

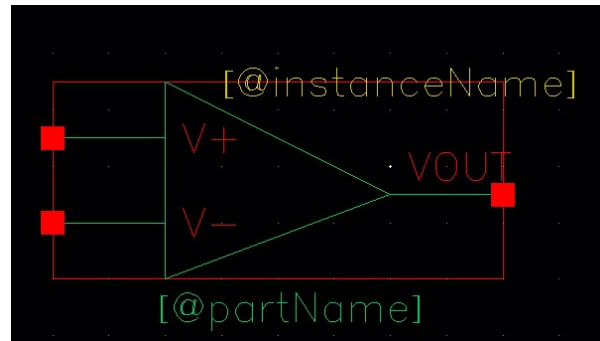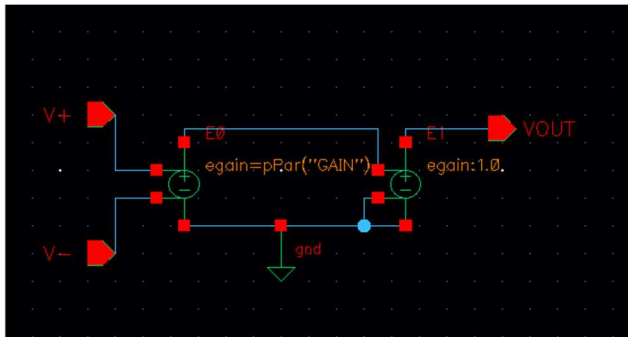


SCHEMATIC:

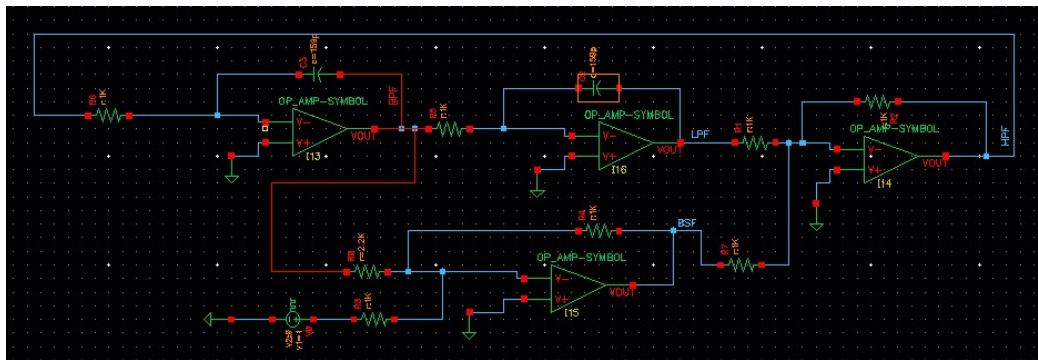


The values of R & C in the schematic are $R=1k\Omega$ & $C=159\text{ PF}$

FREQUENCY RESPONSE:

HPF (MAG PLOT)

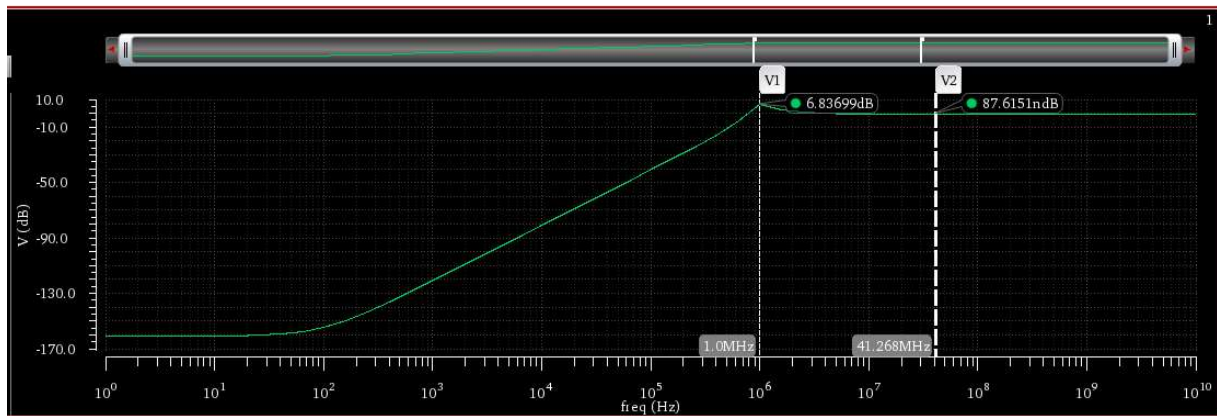

HPF (PHASE PLOT):

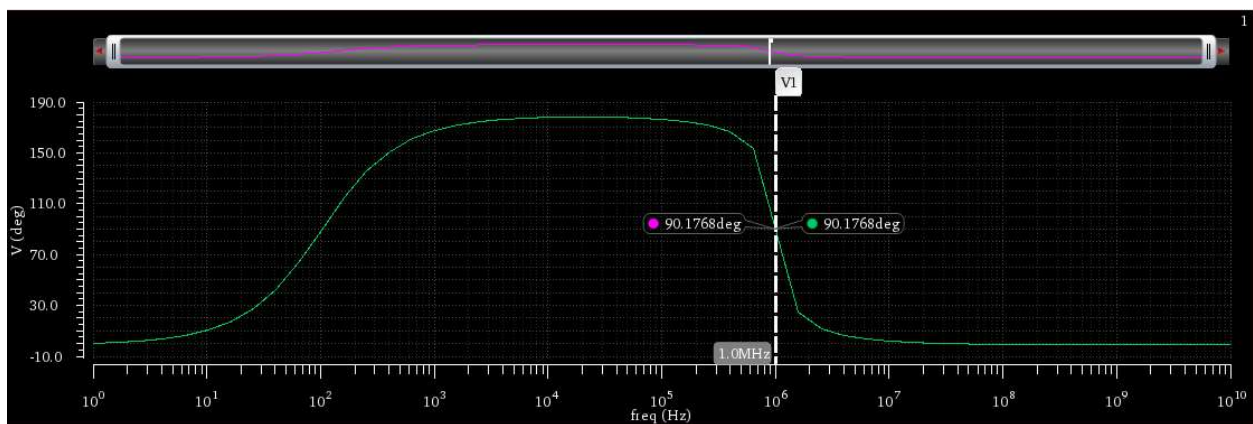

Comments:

- From mag plot we can notice that $f_o = 1 \text{ MHz}$ and $Q = 10^{\frac{6.836}{20}} = 2.196$ (which is the amplitude at ω_o)


$$\text{From HPF TF} = \frac{H_o S^2}{S^2 + \frac{S}{CRQ} + \frac{1}{(CR)^2}} \rightarrow @\omega = 0 \rightarrow \text{TF} = 0$$

$$\rightarrow @\omega = \infty \rightarrow \text{TF} = H_o$$


$$\rightarrow @\omega = \omega_o \rightarrow \text{TF} = QH_o$$

- And V2 cursor show that $H_o = 87.615 \text{ ndB}$ ($\sim 0 \text{ dB}$) at very high frequencies (as it's HPF)

LPF (MAG PLOT):

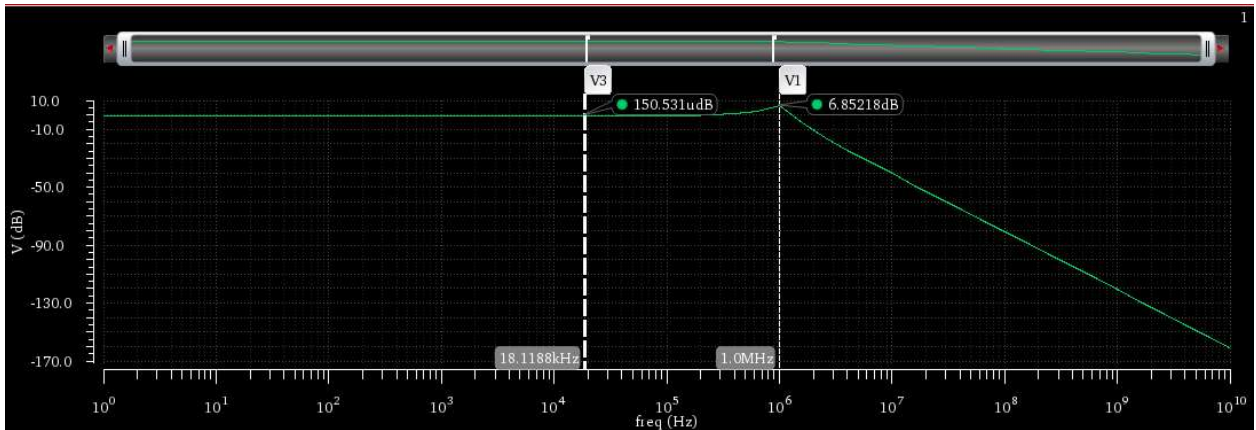


LPF (PHASE PLOT):

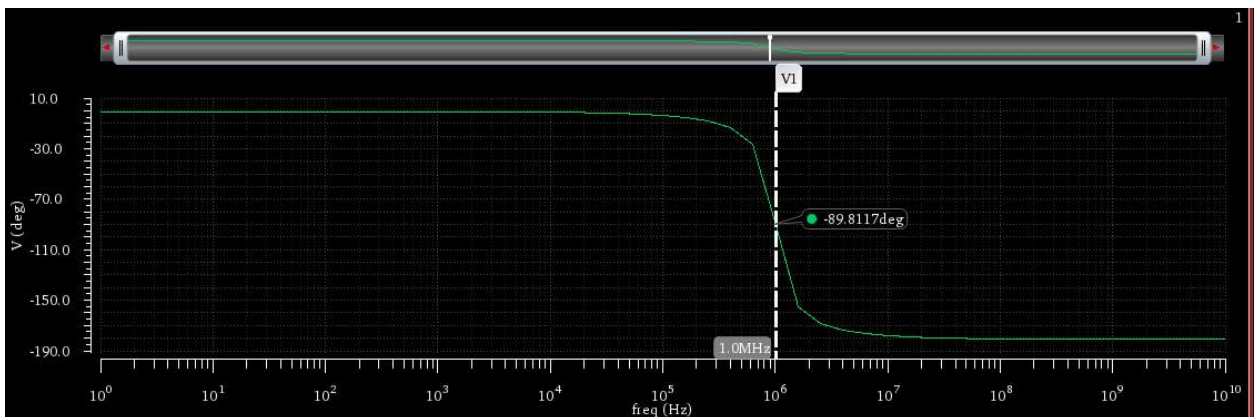


Comments:

- From mag plot we can notice that $f_o = 1 \text{ MHz}$ and $Q = 10^{\frac{6.8521}{20}} = 2.2$ (which is the amplitude at ω_o)
 - From LPF TF = $\left[\frac{\frac{H_o}{(CR)^2}}{S^2 + \frac{S}{CRQ} + \frac{1}{(CR)^2}} \right] \rightarrow @\omega = 0 \rightarrow \text{TF} = H_o$
 - ➔ $@\omega = \infty \rightarrow \text{TF} = 0$
 - ➔ $@\omega = \omega_o \rightarrow \text{TF} = QH_o$
- And V3 cursor show that $H_o = 150.531 \text{ udB}$ ($\sim 0 \text{ dB}$) at low frequencies (as it's LPF)

BPF (MAG PLOT):

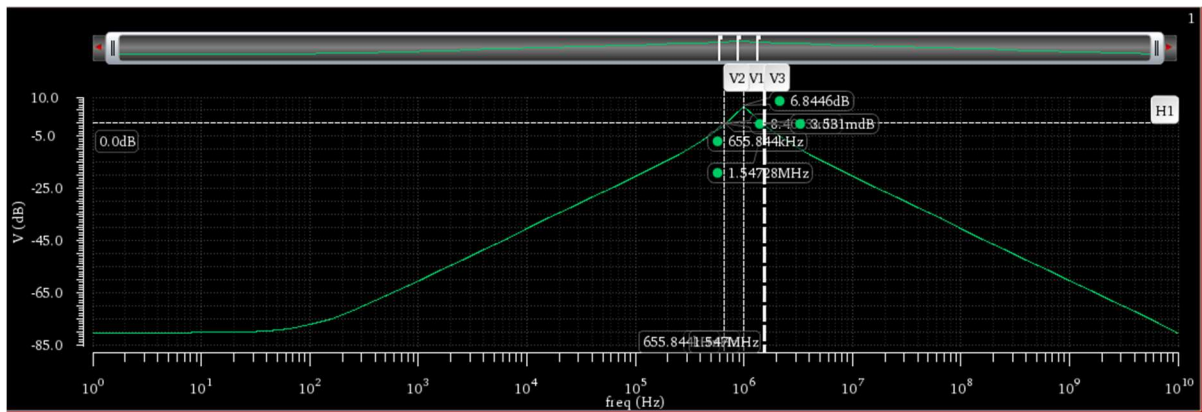


BPF (PHASE PLOT):

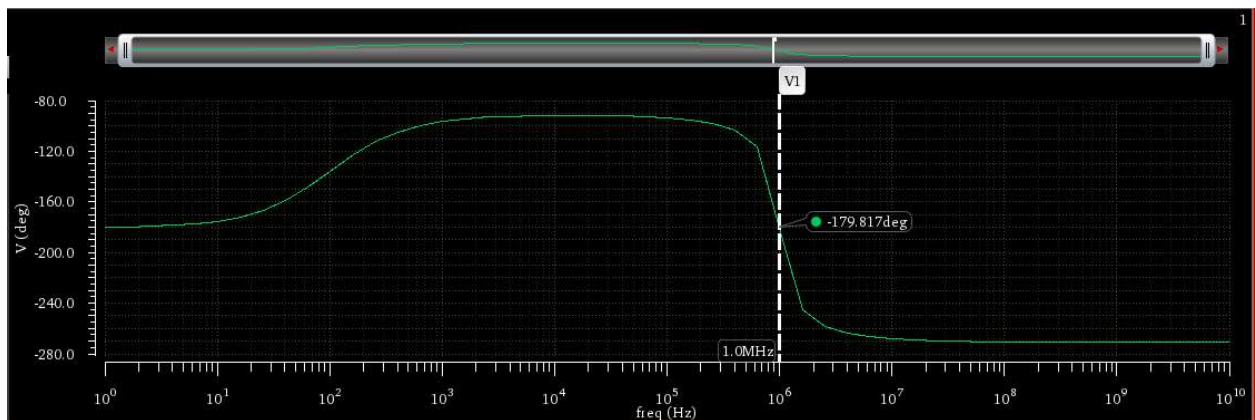


Comments:

- From mag plot we can notice that $f_o = 1 \text{ MHz}$ and $Q = 10^{\frac{6.8446}{20}} = 2.199$ (which is the amplitude at ω_o)
 - From BPF TF = $\left[\frac{\frac{-H}{RC} S}{S^2 + \frac{S}{CRQ} + \frac{1}{(CR)^2}} \right] \rightarrow @\omega = 0 \rightarrow TF = 0$
 - $\rightarrow @\omega = \infty \rightarrow TF = 0$
 - $\rightarrow @\omega = \omega_o \rightarrow TF = QH_o$
- And V2 & V3 cursors show that $H_o \sim 0 \text{ dB}$ at 655.844 kHz to 1.547 MHz (as it's BPF)

BSF (MAG PLOT):

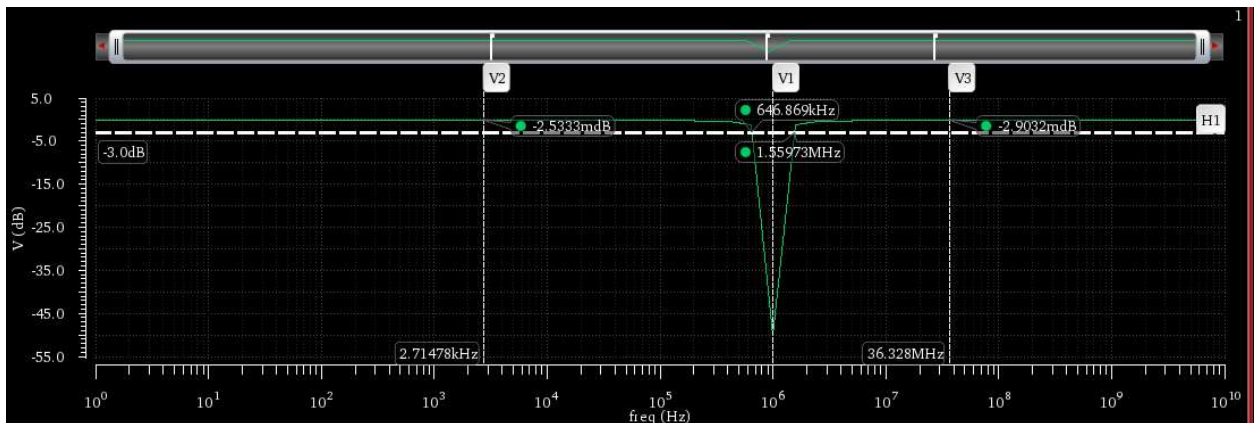

BSF (PHASE PLOT):

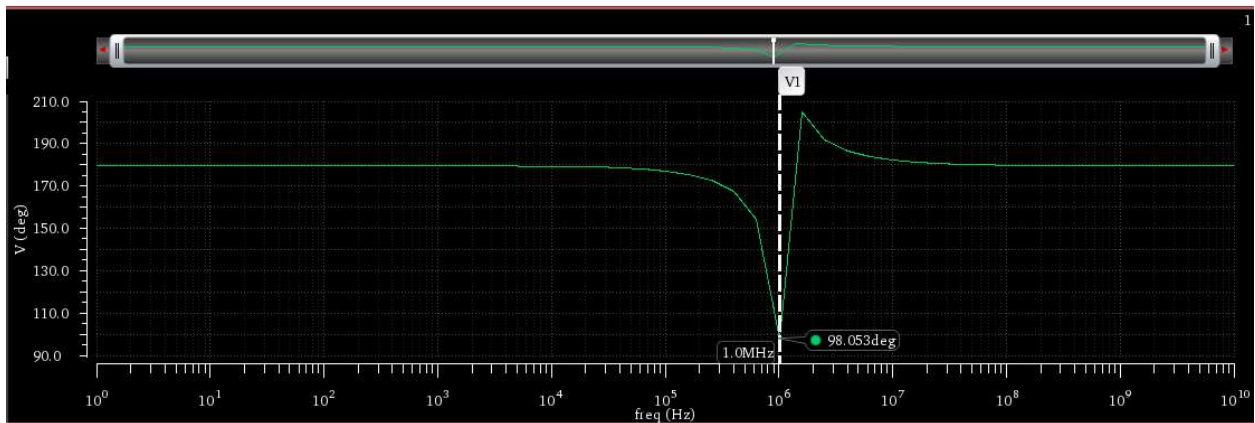


Comments:

- From mag plot we can notice that $f_o = 1 \text{ MHz}$
 - From BSF TF = $-H_o \left[\frac{S^2 + \frac{1}{(CR)^2}}{S^2 + \frac{S}{CRQ} + \frac{1}{(CR)^2}} \right] \rightarrow @\omega = 0 \rightarrow TF = H_o$
 - $\rightarrow @\omega = \infty \rightarrow TF = H_o$
 - $\rightarrow @\omega = \omega_o \rightarrow TF = 0$
- And V2 & V3 cursors show that $H_o \sim 0 \text{ dB}$ at Very low and very high frequencies (as it's BSF)

APPLYING SINE WAVE INPUT


Input sine wave:

Vp-p = 200 mv and Phase = 0

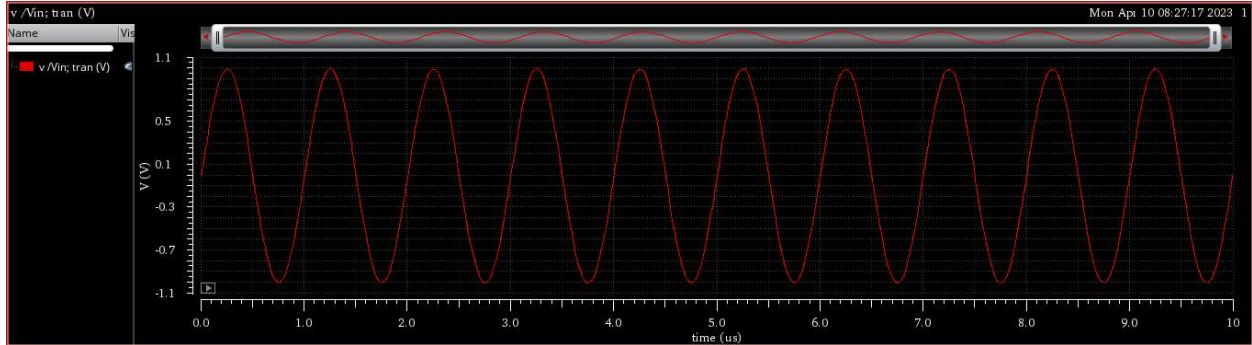


LPF:

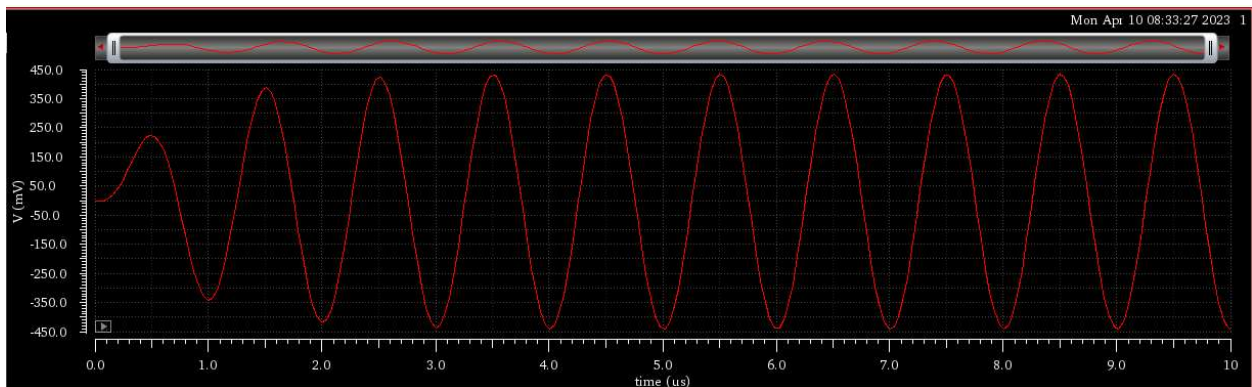Phase of LPF = -90 @ 1MHz and VP-P = 200m * 2.2 = 440 mv and the result phase = -90 (lagging Vin by 90 and HPF by 180)



HPF:

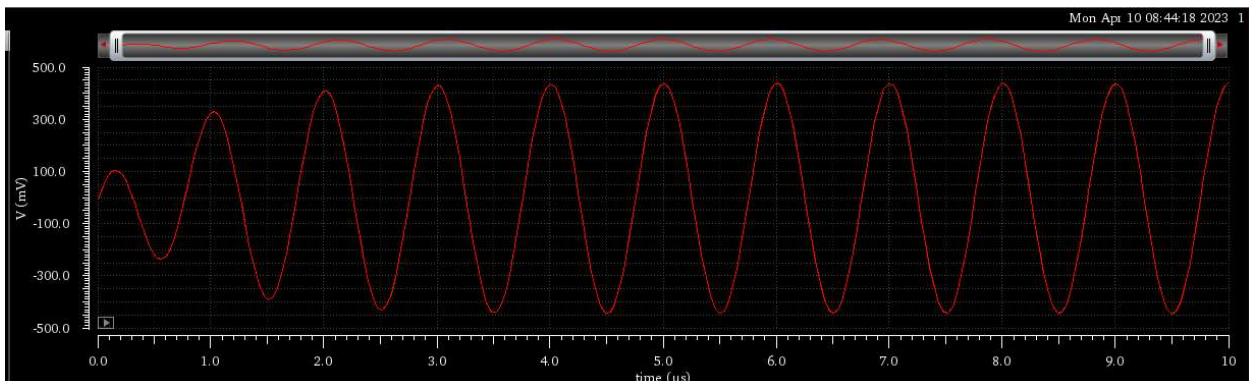Phase of HPF = 90 @ 1MHz and VP-P = 200m * 2.2 = 440 mV and the result phase = 90 (leading Vin by 90 and LPF by 180)



Comments:


- As we applied an input sine wave with 200 mV and frequency 1MHz (cut off frequency of HPF & LPF) And by that they will let the signal pass because VP-P to both of them will be 440mV (which came from multiplying the amplitude of filters at cut off frequency by 200mV)

APPLYING SQUARE WAVE INPUT

BPF:



BSF:

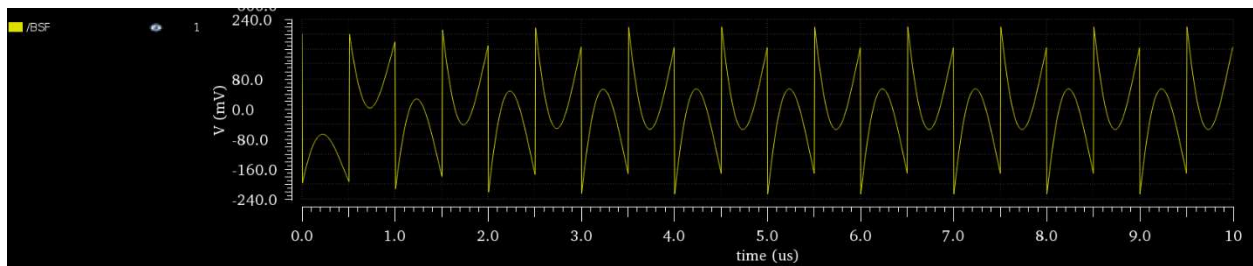

Comments:

From Fourier series we know that square wave is a summation of sines and cosines with many frequencies (harmonics) so at BPF it will let frequency of 1MHz pass and rejects other frequencies so it will appear as sine wave not a square wave as we expected as we see. And for BSF it will stop signal to pass at this

frequency = 1MHz so the signal will appear with distortion and attenuation.